

# Lecture 29, Mar 25, 2022

## Phasors (Continued)

- Phasors are often shown on a phasor diagram on a complex plane, where the length is the magnitude, and the angle is the phase offset
- Alternatively they can be expressed as  $\mathbf{V} = V_m \angle \alpha = V_m e^{j\alpha}$
- Example: Phasor for  $v(t) = V_m \cos(377t + 60^\circ)$  is  $\mathbf{V} = V_m e^{j60^\circ}$ ; phasor for  $i(t) = I_m \sin(377t + 30^\circ)$  is  $\mathbf{I} = I_m e^{-j60^\circ}$ 
  - Note phasors are defined in terms of cosines, which is why  $30^\circ$  becomes  $-60^\circ$
  - Also note how the frequencies don't affect the phasors
- Phasors can be used to add together two sinusoids in frequency domain
- Example: Using phasors, find the sum of  $i_1(t) = 4 \cos(\omega t + 30^\circ)$  and  $i_2(t) = 5 \sin(\omega t - 20^\circ)$ 
  - $\mathbf{I}_1 = 4e^{j30^\circ}$ ,  $\mathbf{I}_2 = 5e^{-j110^\circ}$
  - Convert phasors to rectangular format to add them:  $\mathbf{I}_1 = 4 \cos(30^\circ) + 4j \sin(30^\circ)$ ,  $\mathbf{I}_2 = 5 \cos(-110^\circ) + 5j \sin(-110^\circ)$
  - $\mathbf{I}_1 + \mathbf{I}_2 = 1.754 - 2.698j = 3.218e^{-j56.98^\circ}$

## Derivatives and Integrals of Sinusoids

- $v(t) = V_m \cos(\omega t + \alpha) \implies \mathbf{V} = V_m e^{j\alpha}$
- $\frac{dv}{dt} = -V_m \omega \sin(\omega t + \alpha) = V_m \omega \cos\left(\omega t + \alpha + \frac{\pi}{2}\right)$   
 $\implies \mathbf{V} = V_m \omega e^{j\left(\alpha + \frac{\pi}{2}\right)} = (\omega e^{j\frac{\pi}{2}}) (V_m e^{j\alpha}) = j\omega V_m e^{j\alpha}$
- Taking the time-domain derivative multiplies the phasor by  $j\omega$
- $\int v(t) dt = \frac{V_m}{\omega} \sin(\omega t + \alpha) = \frac{V_m}{\omega} \cos\left(\omega t + \alpha - \frac{\pi}{2}\right) = \frac{1}{j\omega} V_m e^{j\alpha}$   
 $\implies \mathbf{V} = \frac{V_m}{\omega} e^{j\left(\alpha - \frac{\pi}{2}\right)} = \left(\frac{1}{\omega} e^{-j\frac{\pi}{2}}\right) (V_m e^{j\alpha}) = -\frac{j}{\omega} V_m e^{j\alpha}$
- Taking the time-domain integral multiplies the phasor by  $\frac{1}{j\omega}$  (i.e. divide by  $j\omega$ )

## Phasor Relations for R, L, C

- Suppose  $i(t) = I_m \cos(\omega t + \theta_i) \implies \mathbf{I} = I_m e^{j\theta_i}$  passes through a resistor
  - Assuming PSC, by Ohm's law,  $v(t) = Ri(t) = RI_m \cos(\omega t + \theta_i) \implies \mathbf{V} = RI_m e^{j\theta_i} \implies \mathbf{V} = R\mathbf{I}$
- $\mathbf{V} = R\mathbf{I}$  for a resistor; voltage and current are in phase
  - In the phasor diagram, a resistor only changes the length of the phasor and does not rotate it
- For an inductor:  $v(t) = L \frac{di}{dt}$  in the time domain, so in the phasor domain,  $\mathbf{V} = j\omega L\mathbf{I}$ 
  - Since  $j = e^{j90^\circ}$ , an inductor introduces a  $90^\circ$  phase difference (voltage leads current by  $90^\circ$ )
  - The magnitude is scaled by  $\omega L$
  - In the phasor diagram, the two phasors have an angle of  $90^\circ$  relative to each other
- For a capacitor:  $i(t) = C \frac{dv}{dt}$  in the time domain, so in the phasor domain,  $\mathbf{I} = j\omega C\mathbf{V}$  or  $\mathbf{V} = \frac{1}{j\omega C}\mathbf{I}$ 
  - A capacitor also introduces a  $90^\circ$  phase difference (voltage lags current by  $90^\circ$ )